
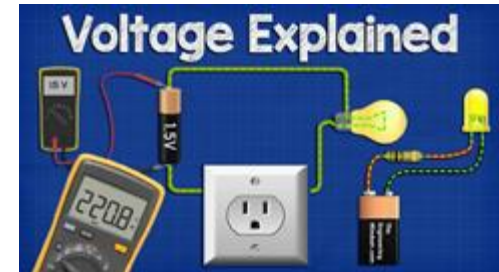



# **EP1000**

**A Short Introduction to Electricity & Electronics**

# What is electricity?

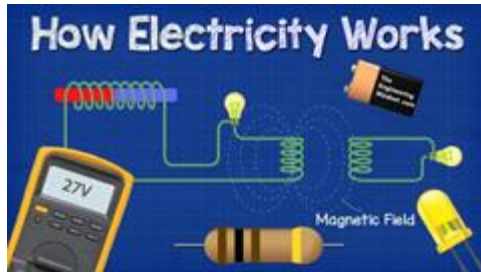

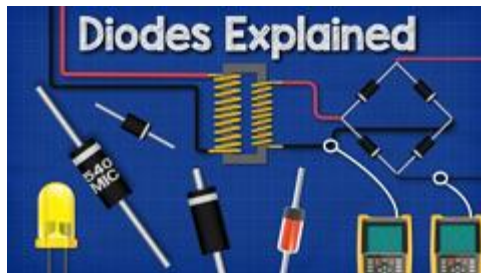
Youtube: The Engineering Mindset  
[Electrical Engineering Basics Playlist](#)


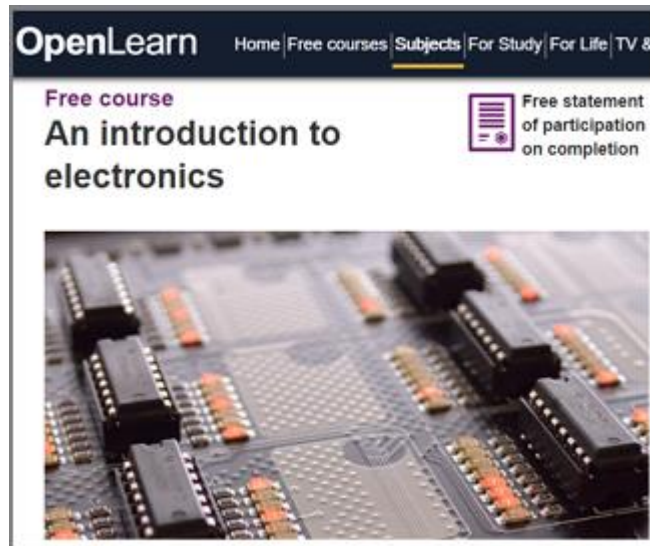
# Electronic Components




YouTube: Great Scott!  
[Essential Electronics Components that you will need for creating projects!](#)



Open University:  
[An Introduction to Electronics](#)

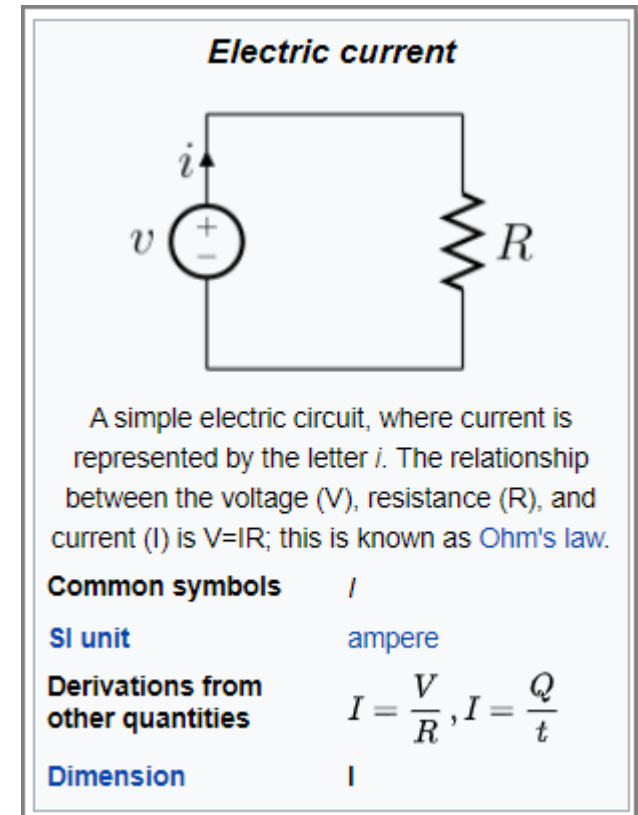
# Electricity

- The **flow** of electrons in a closed circuit.
- **Voltage** is the difference in electrical potential between 2 points (volts)
- **Current** is the rate of flow of electrical charge past a point (amps)
- **Resistance** is a measure of the opposition to the flow of electronics (ohms)


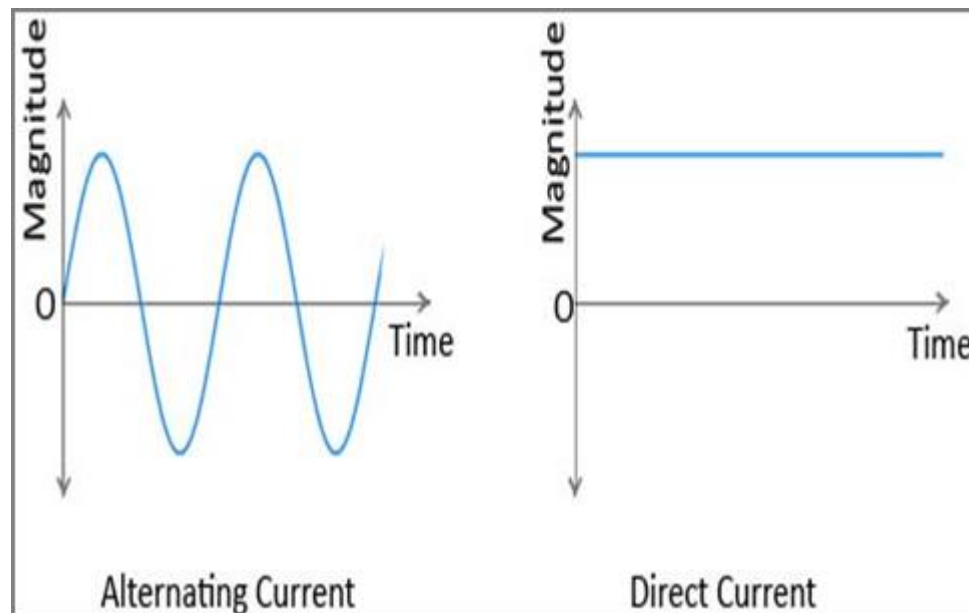
# Types of electrical currents

- Alternating current (AC) where voltage moves from positive to negative values
- E.g. Home electricity
- Direct current (DC) where the potential is at a fixed value
- E.g. Battery



# Ohm's Law


- Voltage = Current \* Resistance

$$V = I R \quad I = \frac{V}{R} \quad R = \frac{V}{I}$$

- Resistance calculation

- Series  $R = R_1 + R_2 + R_3$

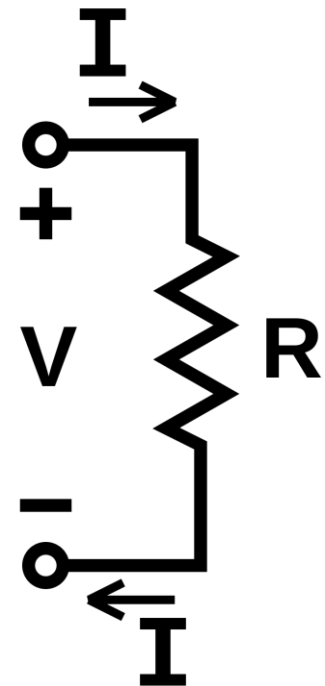- Parallel  $R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$



# Kirchoff's Laws

- Current Law

At any junction, or node, in an electrical circuit, the sum of the currents flowing into the node is the sum of the currents flowing out of a node.

- Voltage Law

When the direction is taken into account, the sum of the potential differences in any closed circuit is zero.

# Electrical components



- Insulators  
Do **NOT** allow current to flow
- Conductors  
Do allow current to flow
- Semiconductors  
Allows current to flow if some electrical conditions are met  
e.g. diodes.




# Common components

- [Wires](#) - [Dupont connector wires](#)
- [Switches](#)
- [Resistors](#) - [Variable resistors](#), potentiometers
- [Capacitors](#)
- [Inductors](#) (seldom used)
- [Diodes](#) - [LED](#) (Light Emitting Diodes)
- Semiconductors - [555 Timer](#), [Voltage Regulators](#)
- Microcontrollers – [Arduino family](#)




YouTube: bigclivedotcom –  
[A Simple Guide to Electronic components](#)

# TinkerCAD

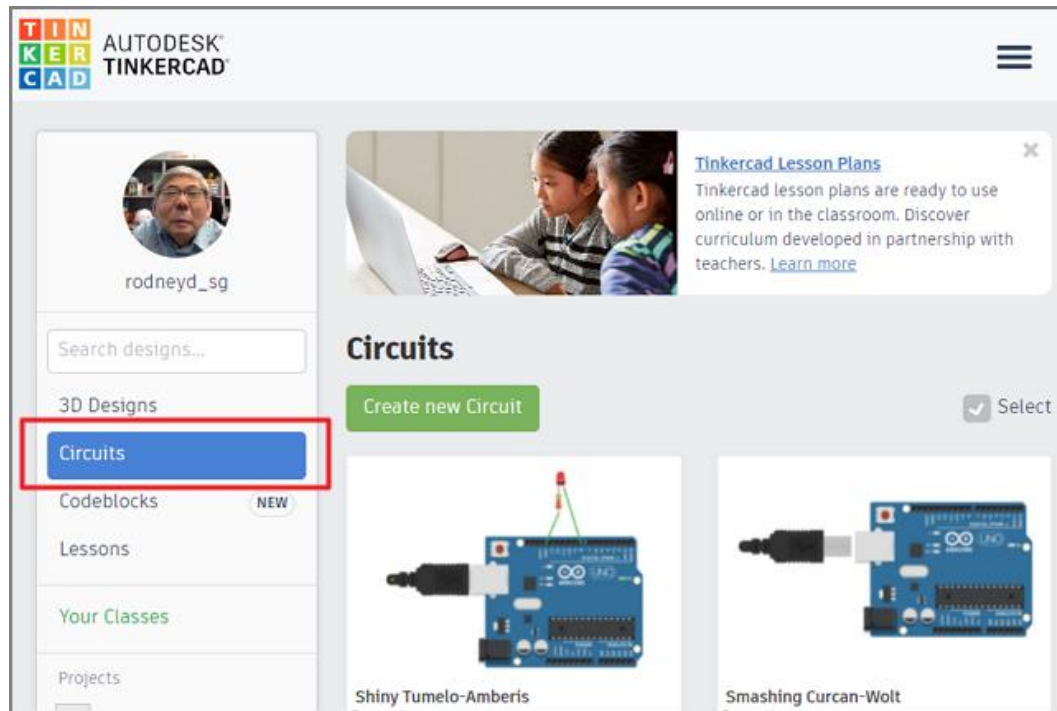


- Allows creation of simple 3D designs
- **Circuits** – allows simulation of
  - Electronic circuits
  - Arduino interfacing with Processing/C++
  - Micro-bit interfacing with CodeBlocks

# Ohms Law

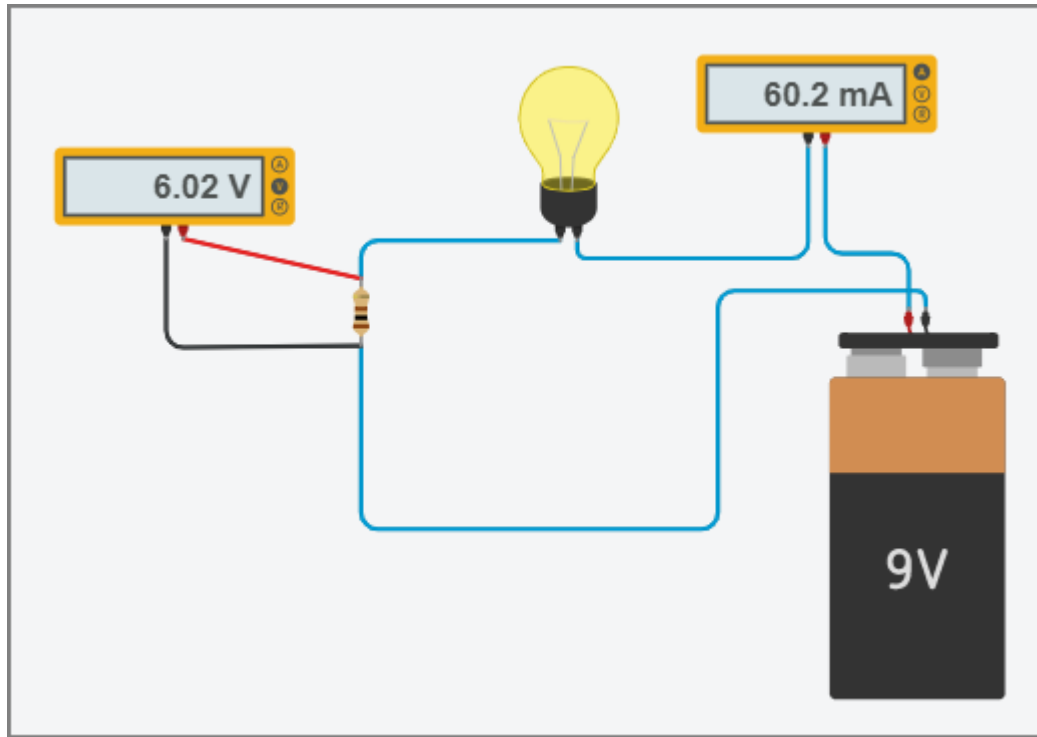


- Change the value of R, check  $V=IR$

# Working with a Breadboard

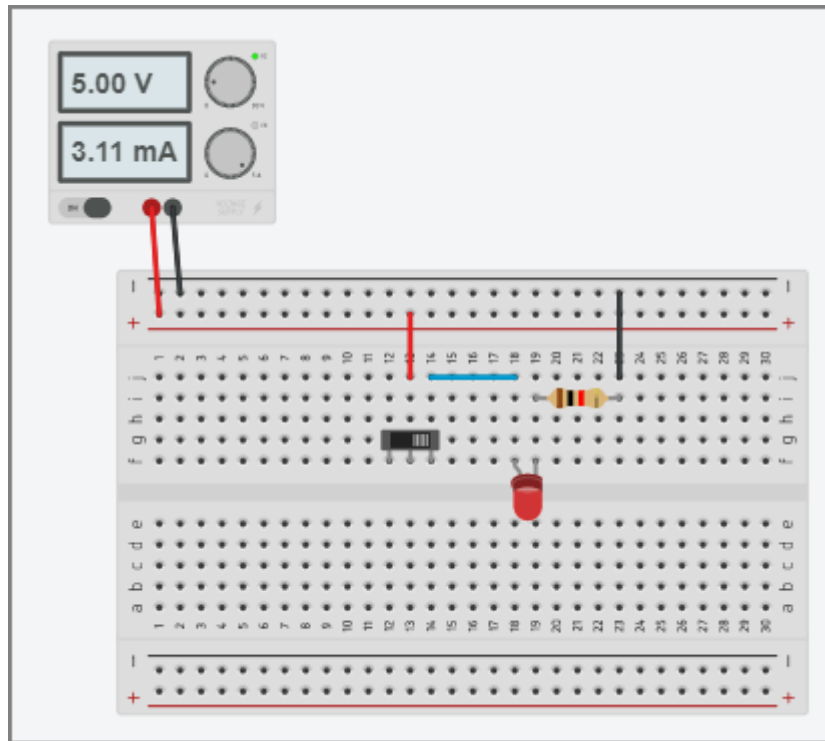


- Breadboard used in many prototyping projects.
- Quick testing of circuits
- Circuit checks effect of R with LED

# Electronic Symbols

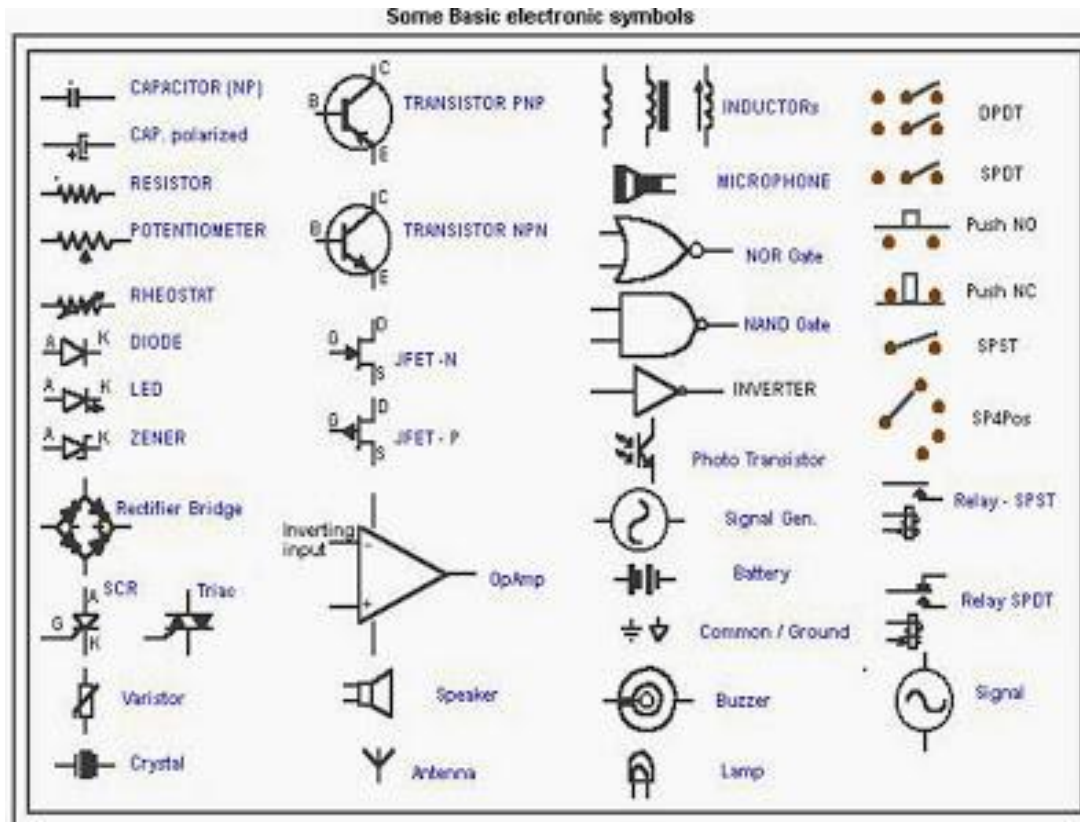


- Provides a short-cut method of drawing/expressing electronics circuits

# LED Circuit

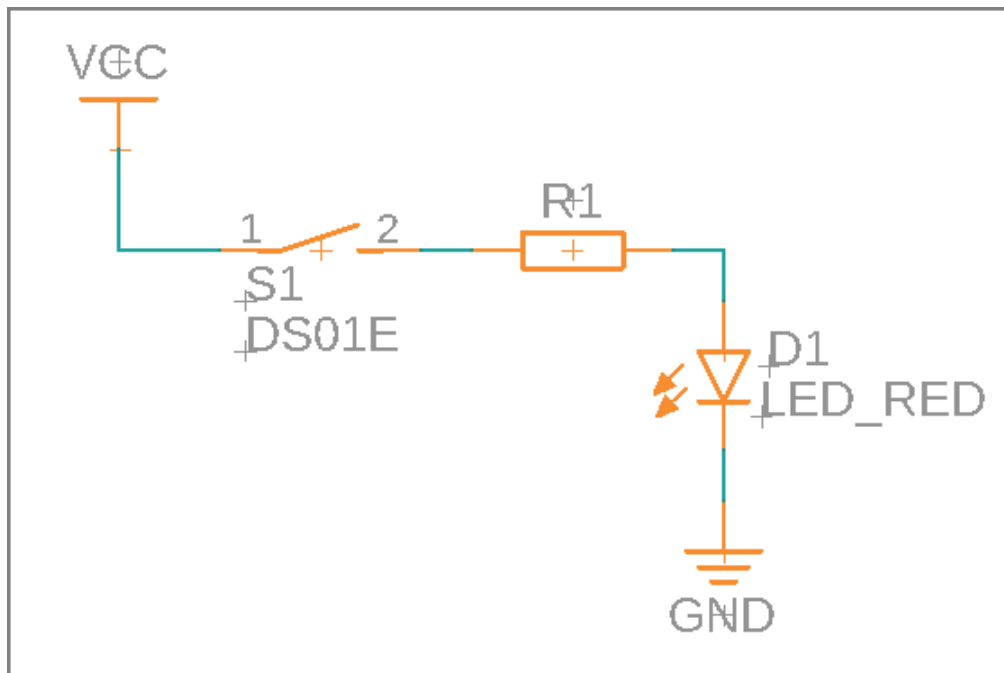


- We use schematics to represent the electrical circuits we create.
- We need to be able to transform from a schematic to a layout and vice versa.

# Assignment

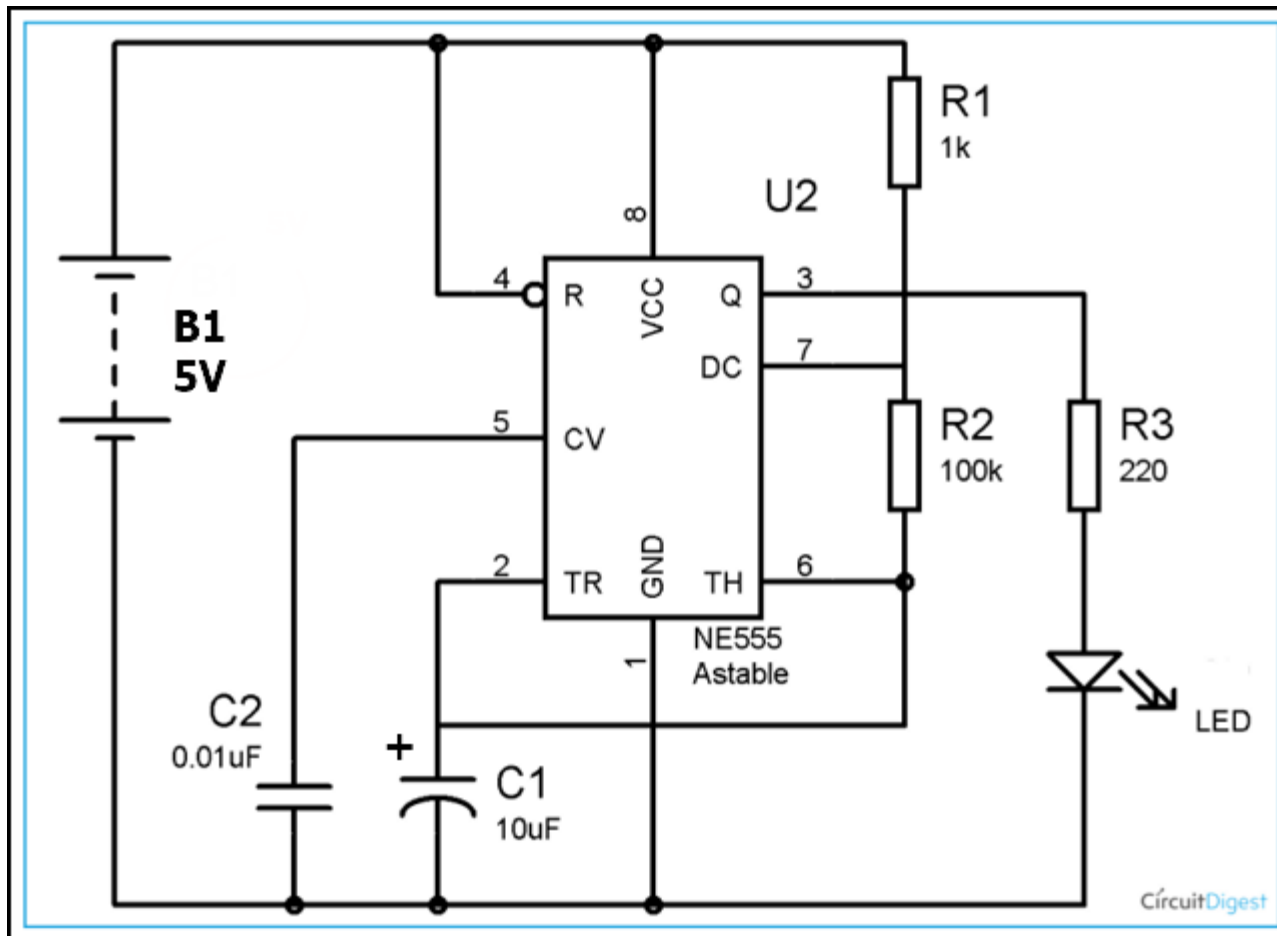

- Convert the schematic into TinkerCAD circuits and simulate it.
- This assignment is **not** graded.

## Expected Result

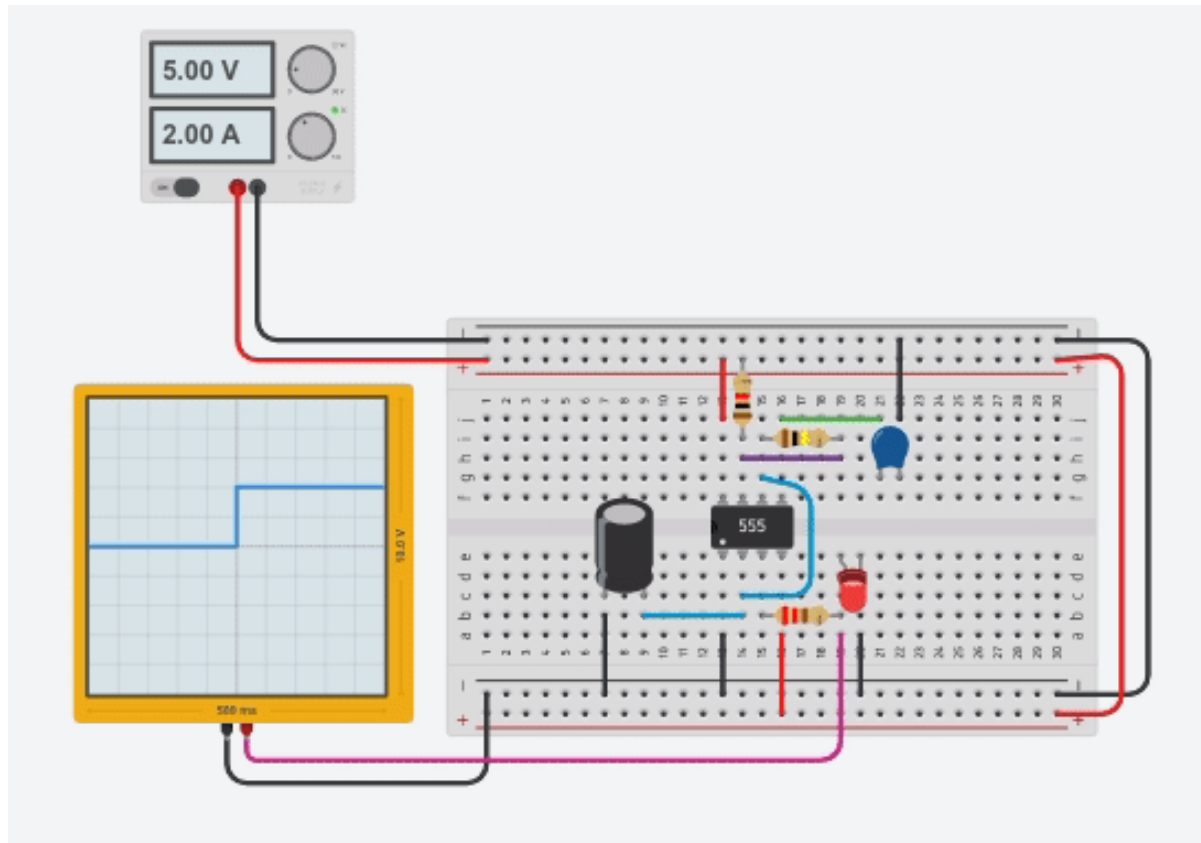

- The 555 timer is configured as an astable using R and C values.
- The result is an alternating ON/OFF signal which flashes the LED



# Hints & Tips

- Assignment sheet: [Electronics](#)
- Good references:
  - [Introduction to TinkerCAD Circuits](#)
  - [Introduction to TinkerCAD Digital](#)
  - [Introduction to Function Generator & Oscilloscope](#)
- You will be asked to implement the circuit on an actual breadboard in the lab.
- Document your experiences

# **EP1000**

**A Short Introduction to Electricity & Electronics**

**End**